



Habib University

EE-172/CS-130/CE-222 Digital Logic and Design - Fall 2021

Instructors: Junaid Memon, Moiz Anis, Owais Talaat, Saad Baig

Time = 120 minutes	Midterm Exam	Max Points: 100
--------------------	--------------	-----------------

Instructions:

- This is an open book, open notes quiz. Students are allowed to use any printed material for reference.
- There are 06 questions in the question paper and all of the questions are mandatory.
- Cell phones, laptops, smart watches, wireless headsets or any other electronic gadgets except scientific calculators are prohibited to use during the exam.
- The question paper **must be returned** at the end of the exam along with the answer script.
- Give proper reasoning to your questions where required. Ambiguous answers or untidy work will result in the deduction of your points.
- Answer sheets should contain **all working and explanations** and assumptions.

CLO Assessment:

This assignment assesses students for the following course learning outcomes.

Course Learning Outcomes		CLO Assessed
CLO 1	Apply r-base (binary, octal, decimal, hexadecimal numbers systems) to digital systems and carry out arithmetic operations and conversions	✓
CLO 2	Apply principles of Boolean Algebra to represent and build equivalent realizations of digital logic (circuits)	✓
CLO 3	Design combinational logic circuits using logic gates	✓
CLO 4	Design sequential systems using finite state machine methodology	

Exam Paper

Number Systems (CLO 01)

Question 1: (15 marks) [Expected time 15 mins]

Suppose that you are in a special task force team that is given a task to create a watch that tells you time in minutes 0-59 mins, but no one except your team should be able to read it. You are required to use all of the following characters only (no other characters are allowed):

Coded Symbols

@	#	\$	%	+	&	<	>
---	---	----	---	---	---	---	---

- (a) (05 marks) Fill in the following table and state your assumptions (4 marks)
- (b) (05 marks) Represent 43_{10} minutes in your coded notation (3 marks)
- (c) (05 marks) In your number system what does (\$@#) represents in decimal?

Actual	0	1	2	3	4	5	6	7	8	9	10	11	12
Coded													

Question 2: (15 marks) [Expected time 15 mins]

Do the following arithmetic operation in binary. Determine if the result is correct or not and indicate if there is overflow in the result. Use 2's complement format where required.

- (a) (3 marks) 8-bit unsigned operation: $(91) + (57)$
- (b) (3 marks) 8-bit signed operation: $(91) + (57)$
- (c) (3 marks) 8-bit signed operation: $(19) - (75)$
- (d) (3 marks) 8-bit BCD addition: $(19) + (75)$
- (e) (3 marks) 8-bit BCD subtraction: $(19) - (75)$

Note: You can skip comment on overflow in part (d) & (e).

Boolean Algebra and Minimization (CLO 02)

Question 3: (15 marks) [Expected time 15 mins]

Obtain the 2-level NOR implementation and draw the circuit diagram for the following function:

$$F = [(A+B'+C)(AB+C')]'$$

Note: You have both complemented and uncomplemented types of inputs available.

Question 4:(25 marks) [Expected time 20 mins]

A 2-bit-wide shifter takes two input signals, i_0 and i_1 , and shifts them to two outputs, o_0 and o_1 , under the control of a shift signal S . If S is false, then the outputs are equal to their corresponding inputs. If S is true, then o_1 is equal to i_0 and o_0 is set to 0.

- (10 marks) Complete the following truth table
- (05 marks) Write down the *Canonical POS* expression for the above outputs.
- (10 marks) Use k-maps to find the most simplified PoS expression for both outputs.

Sample Truth Table

S	i_0	i_1	o_0	o_1
0	0	1	0	1
1	1	0	0	1

Combinational Logic Circuits (CLO 03)

Question 5: (30 marks) [Expected time 30 mins]

A student team arranges a limited inventory by pooling the funds. They are required to develop **two different** circuits of a 2-bit Magnitude differentiator (defined below), to be used in different parts of the robotic limbs of their prototype. Inventory parts, their quantity and cost is given as under.

A magnitude differentiator is a system which provides output D as the magnitude of difference between two numbers (A and B) i.e.

$$D = |A - B|$$

Inventory of Items

Type of part	Quantity available	Price per part
16 x 1 MUX	2	Rs. 100
8 x 1 MUX	4	Rs. 40
4 x 1 MUX	8	Rs. 12
AND/OR/NOT gates	5 DIP ICs (20 gates) for each type	Rs. 12 per IC (4 gates per IC)
3 x 8 Decoder	2	Rs. 30
Full Adders	2	Rs. 50
XOR gates	1 DIP IC (4 gates)	Rs. 20 per IC

- (05 marks) Complete the following truth table.
- (05 marks) Write down the boolean function to describe the function D.
- (05 marks) List down atleast 04 possible different implementations of the logic regardless of cost.
- (10 marks) Pick the items from given inventory and rearrange the expression or use simplification methods to show two different implementations of the logic.
- (05 marks) Comment on approach to get least possible expense and least possible gate delay.

Sample Truth Table

A		B		D	
A1	A0	B1	B0	D1	D0
:	:	:	:	:	:
0	0	0	1	0	1
:	:	:	:	:	:
1	1	1	0	0	1
:	:	:	:	:	:

----- END OF PAPER -----