


Dated: DLD Assignment #4

Ali Muhammad ibad
aa07190

624

Iqra Ahmed

ia07674 L2

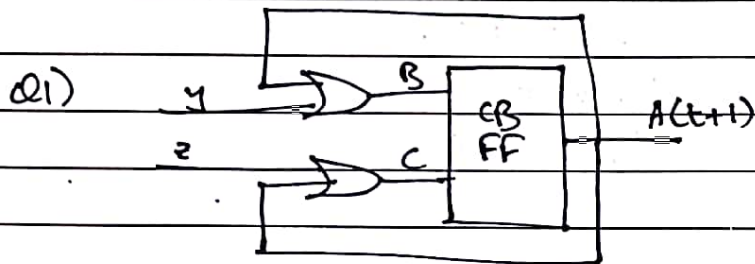

- i) $BC = 11$, 0
- ii) $BC = 10$, Comp
- iii) $BC = 01$, 1
- iv) $BC = 00$, No change

(a) Characteristic Table

B	C	$A(t+1)$
1	1	0
1	0	$A'(t)$
0	1	1
0	0	$A(t)$

(b)

$A(t)$	B	C	$A(t+1)$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$A(t)$	BC	00	01	11	10
0		0	1	0	1
1		1	1	0	0

$$A(t+1) = A(t)B' + 0B'C + A(t)'BC'$$

(c) Excitation Table

$A(t)$	$A(t+1)$	B	C
0	0	x	x
0	1	x	x
1	0	1	x
1	1	0	x

- * $A(t) = 0$ & $A(t+1) = 0$, $B = 0$ & 1, $C = 0$ & 1
- * $A(t) = 0$ & $A(t+1) = 1$, $B = 0$ & 1, $C = 0$ & 1
- * $A(t) = 1$ & $A(t+1) = 0$, $B = 1$, $C = 0$ & 1
- * $A(t) = 1$ & $A(t+1) = 1$, $B = 0$, $C = 0$ & 1

Dated:


d) State Transition Table

Present State Previous State	Inputs	Next State	Output
$A(t)$	$y \quad z$	$A(t+1)$	$B \quad C$
0	0 0	0	0 0
0	0 1	1	0 1
0	1 0	1	1 0
0	1 1	0	1 1
1	0 0	0	1 1
1	0 1	0	1 1
1	1 0	0	1 1
1	1 1	0	1 1

Dated:

(22) id: aia07674

(a)

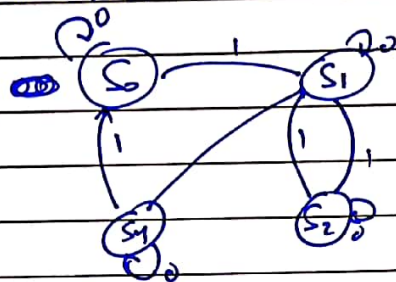

$S_0 = 000$

$S_1 = 111$

$S_2 = 110$

$S_3 = 111$

$S_4 = 010$

} Same (S_1 & S_3)

(b) Present State Input Next State
 $A_3 \ A_2 \ A_1 \ A_0$ I $A_3 \ A_2 \ A_1 \ A_0 (t+1)$

0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	1	1	1
0	1	1	1	1	0	1	1	0
0	1	1	0	1	0	1	1	1
0	1	1	1	1	0	0	1	0
0	0	1	0	1	0	0	0	0
0								

(c)

$A_2(t+1) :$

		$A_1 A_0$			
		00	01	11	10
A_3	00	1	x	x	0
	01	x	x	x	1
	11	x	x	x	x
	10	x	x	x	x

$b(t+1)$

		$A_1 A_0$			
		00	01	11	10
A_3	00	1	x	x	0
	01	x	x	0	1
	11	x	x	x	x
	10	x	x	x	x

A_3 is always 0

$$A_2(t+1) = A_1' + A_2$$

$$A_0(t+1) = A_1' + A_2 A_0'$$


$A_1(t+1)$

		$A_1 A_0$			
		00	01	11	10
A_3	00	1	x	x	0
	01	x	x	1	1
	11	x	x	x	x
	10	x	x	x	x

$$A_1(t+1) = A_1' + A_2$$

Dated:

Q3)

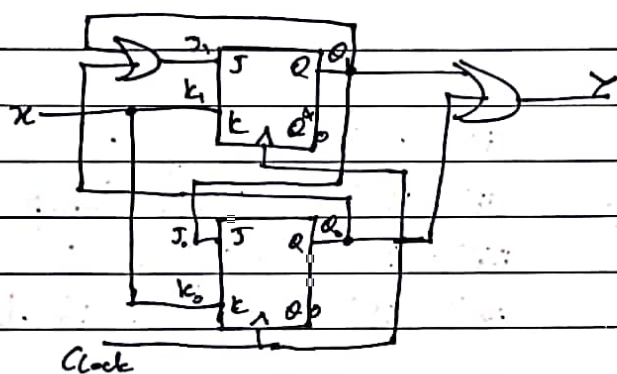

$$J_0 = Q_1$$

$$K_0 = x$$

$$J_1 = Q_0 + Q_1$$

$$K_1 = x$$

$$Y = Q_0 + Q_1$$

(a) Excitation Equations:

$$J_0 = Q_1, K_0 = x, J_1 = Q_0 + Q_1, K_1 = x$$

$$Y = Q_0 + Q_1 \rightarrow \text{Output Equation}$$

A

Transition Equation:

$$Q_1(t+1) = J_1 Q_1(t)' + K_1' Q_1(t)$$

$$\Rightarrow J_1 = Q_0 + Q_1, K_1 = x$$

$$Q_1(t+1) = (Q_0 + Q_1) Q_1(t)' + x' Q_1(t)$$

$$= Q_0 Q_1(t)' + Q_1 Q_1(t)' + x' Q_1(t)$$

$$Q_1(t+1) = Q_0 Q_1(t)' + x' Q_1(t)$$

$$Q_0(t+1) = Q_0(t)' J_0 + K_0' Q_0 \quad [J_0 = Q_1, K_0 = x]$$


$$Q_0(t+1) = Q_0(t)' Q_1 + x' Q_0$$

(b) Present State		Input x	Next State		Flip Flop Input				Output Y
Q_1	Q_0		Q_1	Q_0	J_1	K_1	J_0	K_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	1	0
0	1	0	1	1	1	0	1	0	1
0	1	1	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1	0	1
1	0	1	0	1	1	1	1	1	1
1	1	0	1	1	1	0	1	0	1
1	1	1	0	0	1	1	1	1	1

Q3

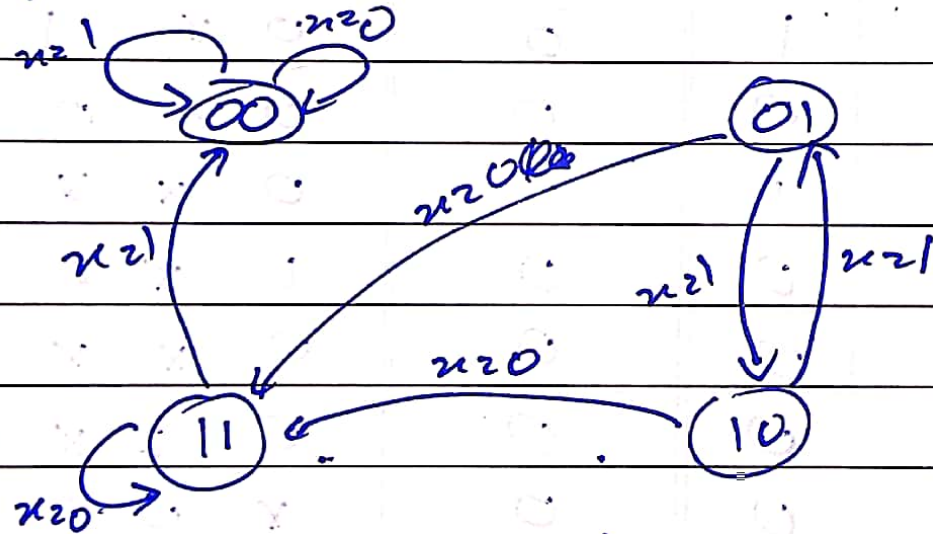(c) State Diagram:

2 inputs define state \Rightarrow 2 bits, 4 states



This is clearly a Moore Machine as output is only dependent on the present state.

4a.

CLK

J

K

Q


4b.

S

R

Q

4c.

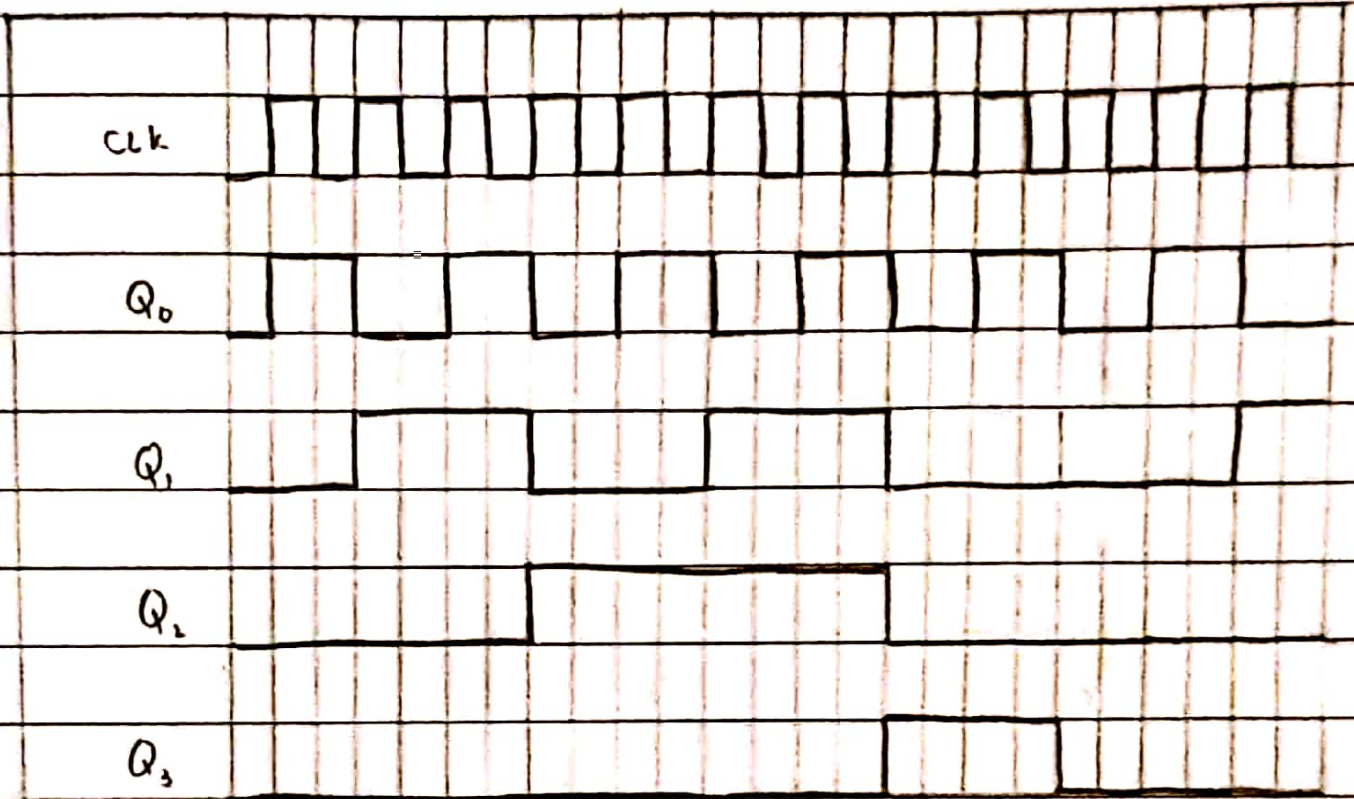

Asynchronous BCD counter

5.

a.

Present State	Next State		Output	
	$x=0$	$x=1$	$x=0$	$x=1$
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0


b. b and e are equivalent

d and h are equivalent

because same output and next state as shown in table

	Present State	Next State		Output	
		$x=0$	$x=1$	$z=0$	$z=1$
	a	f	b	0	0
	b	d	c	0	0
	c	f	b	0	0
	d	g	a	1	0
	f	f	b	1	1
	g	g	d	0	1

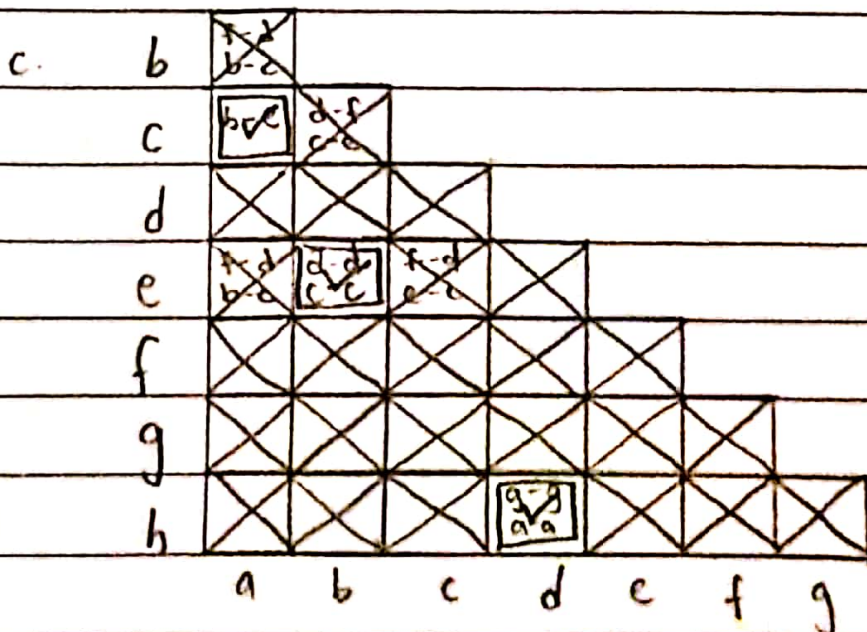
a and c are equivalent so one can be removed from table (updated table shown in next page).



b (on/d)	Present State	Next State		Output	
		x=0	x=1	x=0	x=1
	a	f	b	0	0
	b	d	a	0	0
	d	g	a	1	0
	f	f	b	1	1
	g	g	d	0	1

No more equivalent states can be deduced from table

d.

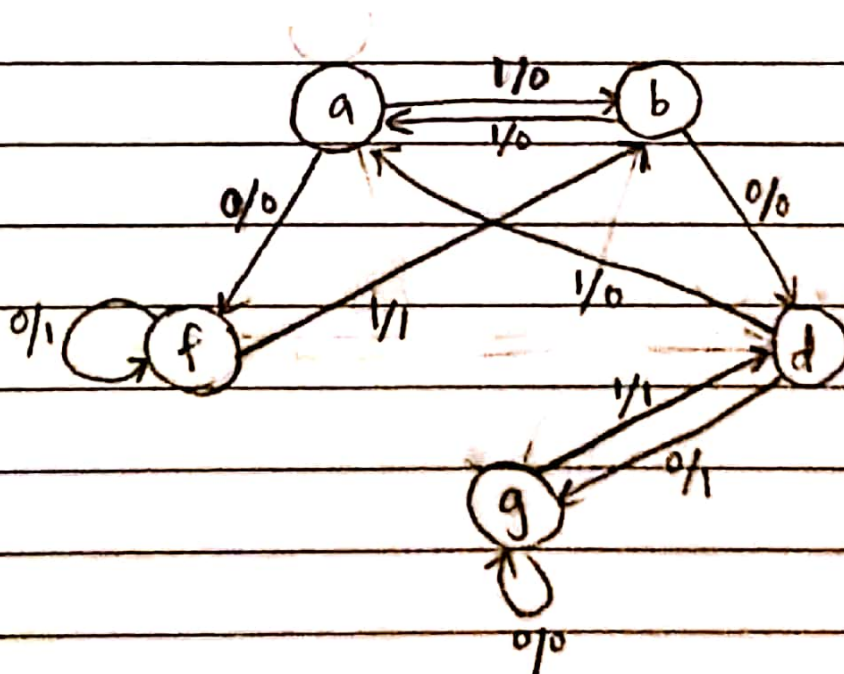


Dated:

Q6) JK FF & 'DLD' → input → pins lab.

Inputs: D & L, output X

2 bits, 4 States

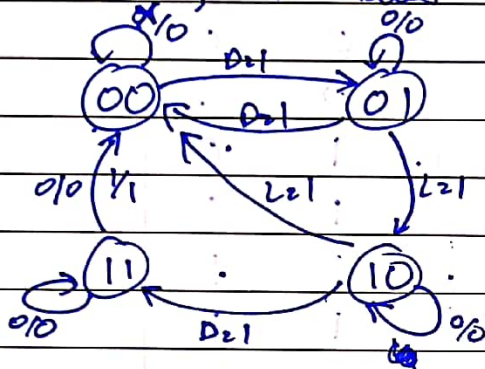

$S_0 = 00$: Idle

$S_1 = 01$: D

$S_2 = 10$: L

$S_3 = 11$: D

State Table:

Present State		Inputs		Next State		Output X	JK Flip Flop			
A	B	D	L	A(t+1)	B(t+1)		J _A	K _A	J _B	K _B
0	0	0	0	0	0	0	0	x	0	x
0	0	0	1	0	0	0	0	x	0	x
0	0	1	0	0	1	0	0	x	1	x
0	0	1	1	0	0	0	0	x	0	x
0	1	0	0	0	1	0	0	x	x	0
0	1	0	1	1	0	0	1	x	x	1
0	1	1	0	0	0	0	0	x	x	1
0	1	1	1	0	0	0	0	x	x	0
1	0	0	0	1	0	0	x	0	0	x
1	0	0	1	0	0	0	x	1	0	x
1	0	1	0	1	1	0	x	0	1	x
1	0	1	1	0	0	0	x	0	0	x
1	1	0	0	1	1	1	x	0	x	0
1	1	0	1	0	0	1	x	1	x	1
1	1	1	0	0	0	1	x	1	x	1
1	1	1	1	0	0	1	x	1	x	1

Dated:

J_A :

AB \ D	00	01	11	10
00	0	0	0	0
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

A { 11, 10 } B { 01, 11, 10 }

K_A :

AB \ D	00	01	11	10
00	x	1	x	x
01	x	1	1	1
11	0	1	1	1
10	0	1	0	0

A { 11, 10 } B { 01, 11, 10 }

~~$J_A = BD'L$~~

$K_A = BD + D'L$

J_B :

AB \ D	00	01	11	10
00	:	:	:	1
01	x	x	x	x
11	x	x	x	x
10			0	1

A { 11, 10 } B { 01, 11, 10 }

K_B :

AB \ D	00	01	11	10
00	x	1	x	1
01		1		1
11		1	1	1
10	1	1	1	1

A { 11, 10 } B { 01, 11, 10 }

$J_B = DL'$

$K_B = D'L + DL' + AL$

$K_B = (D \oplus L) + AL$

X :

AB \ D	00	01	11	10
00				
01				
11	1	1	1	1
10				

A { 11, 10 } B { 01, 11, 10 }

$X = AB$

$J_A = BD'L$

$K_A = BD + D'L$

$J_B = DL'$

$K_B = (D \oplus L) + AL$

$X = AB$

Dated:

$$J_A = BD'L$$

$$K_A = BD + D'L$$

$$J_B = DL'$$

$$K_B = (D \oplus L) + AL$$

$$\text{Output : } X = AB$$

